

# VLSI PRACTICE QUESTIONS SOLUTION

Done By T Tushar Shenoy

**NOTE:-**Add Compiler Directives as given in Lab Manual if in case they mention, also make sure you know about Tasks and Repeat functions, They may ask to draw the Block Diagram of the Verilog and Testbench Code.

- 1) Verilog codes for logic operations on 3 or more input bits, Verilog gate level model for a given Boolean expression and relevant Verilog testbenches.

## Verilog Code

```
module logic_gates_3in(a,b,c,yor,yand,ynor,ynand,yxor,yxnor);  
input a,b,c;  
output yor,yand,ynor,ynand,yxor,yxnor;  
  
or(yor,a,b,c);  
and(yand,a,b,c);  
nor(ynor,a,b,c);  
nand(ynand,a,b,c);  
xor(yxor,a,b,c);  
xnor(yxnor,a,b,c);  
  
endmodule
```

## Testbench

```
module logic_gates_3in_tb;

reg a,b,c;

wire yor,yand,ynor,ynand,yxor,yxnor;


logic_gates_3in
dut(.a(a),.b(b),.c(c),.yor(yor),.yand(yand),.ynor(ynor),.ynand(ynand),.
yxor(yxor),.yxnor(yxnor));

initial begin

repeat(10)
begin
a=$random;
b=$random;
c=$random;
#5;
end
$finish;
end

endmodule
```

## OUTPUT WAVEFORM

 

Consider the Expression  **$Y=AB+CD+ABCD$**

### Verilog Code

```
module logic_expression(a,b,c,d,y);
```

```
//Consider y=ab+cd+abcd
```

```
input a,b,c,d;
```

```
output y;
```

```
wire w1,w2,w3;
```

```
and(w1,a,b);
```

```
and(w2,c,d);
```

```
and(w3,a,b,c,d);
```

```
or(y,w1,w2,w3);
```

```
endmodule
```

## TESTBENCH

```
module logic_expression_tb;  
reg a,b,c,d;  
wire y;  
logic_expression dut(.a(a),.b(b),.c(c),.d(d),.y(y));
```

```
initial begin
```

```
repeat(10)
```

```
begin
```

```
  a=$random;
```

```
  b=$random;
```

```
  c=$random;
```

```
  d=$random;
```

```
  #5;
```


```
end
```

```
  $finish;
```

```
end
```

```
endmodule
```

## OUTPUT WAVEFORM

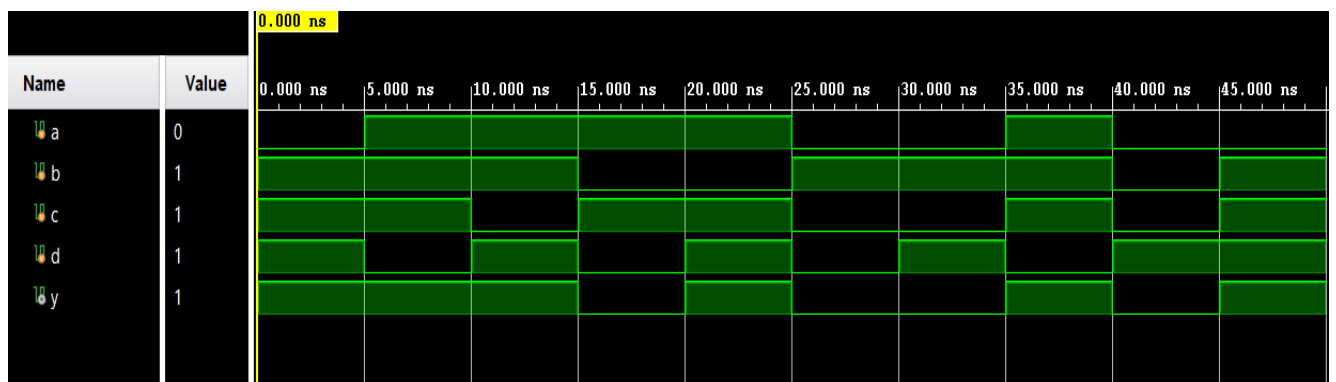

2) Verilog code to compute 2's complement of a nibble data. Write relevant Verilog testbenches


### **Verilog Code**

```
module nibble_2s_complement(  
    input [3:0]data_in,  
    output [3:0]data_out  
);  
    assign data_out=~(data_in)+1'b1;  
endmodule
```

## Testbench

```
module nibble_2s_complement_tb();  
reg [3:0]data_in;  
wire [3:0]data_out;  
  
nibble_2s_complement dut(.data_in(data_in),.data_out(data_out));  
  
initial begin  
    repeat(25)  
        begin  
            data_in=$random;  
            #5$display("The Input Nibble is Data_in=%b and the 2's  
Complemented Output is Data_out=%b",data_in,data_out);  
            #5;  
        end  
    $finish;  
end  
endmodule
```

## OUTPUT WAVEFORM

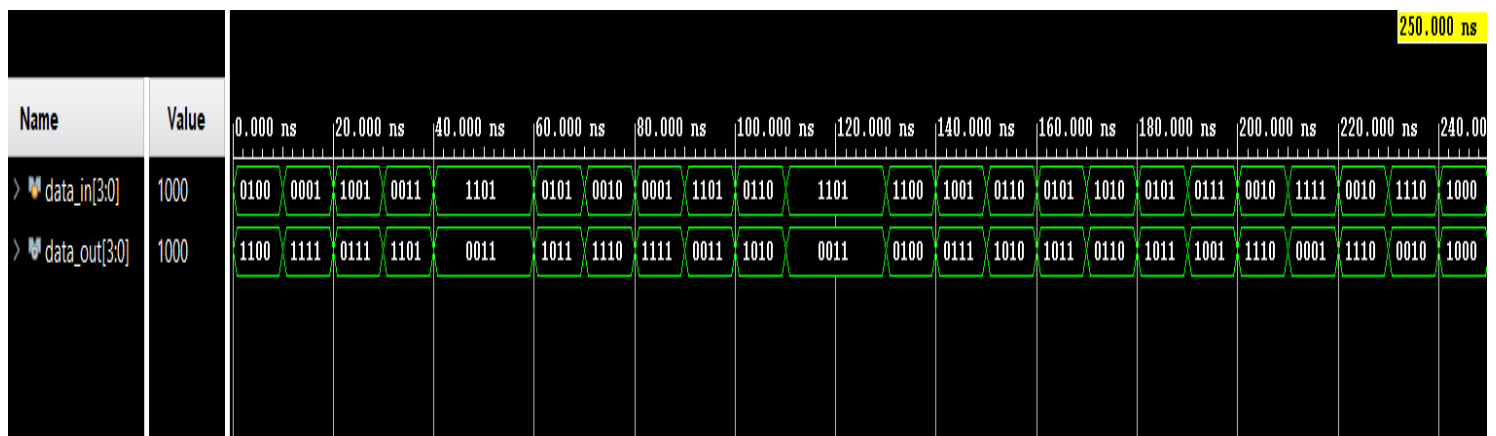

# CONSOLE OUTPUT

Tcl Console x Messages Log

The Input Nibble is Data\_in=0001 and the 2's Complementated Output is Data\_out=1111  
The Input Nibble is Data\_in=1001 and the 2's Complementated Output is Data\_out=0111  
The Input Nibble is Data\_in=0011 and the 2's Complementated Output is Data\_out=1101  
The Input Nibble is Data\_in=1101 and the 2's Complementated Output is Data\_out=0011  
The Input Nibble is Data\_in=1101 and the 2's Complementated Output is Data\_out=0011  
The Input Nibble is Data\_in=0101 and the 2's Complementated Output is Data\_out=1011  
The Input Nibble is Data\_in=0010 and the 2's Complementated Output is Data\_out=1110  
The Input Nibble is Data\_in=0001 and the 2's Complementated Output is Data\_out=1111  
The Input Nibble is Data\_in=1101 and the 2's Complementated Output is Data\_out=0011  
The Input Nibble is Data\_in=0110 and the 2's Complementated Output is Data\_out=1010  
The Input Nibble is Data\_in=1101 and the 2's Complementated Output is Data\_out=0011  
The Input Nibble is Data\_in=1101 and the 2's Complementated Output is Data\_out=0011  
The Input Nibble is Data\_in=1100 and the 2's Complementated Output is Data\_out=0100  
The Input Nibble is Data\_in=1001 and the 2's Complementated Output is Data\_out=0111  
The Input Nibble is Data\_in=0110 and the 2's Complementated Output is Data\_out=1010  
The Input Nibble is Data\_in=0101 and the 2's Complementated Output is Data\_out=1011  
The Input Nibble is Data\_in=1010 and the 2's Complementated Output is Data\_out=0110  
The Input Nibble is Data\_in=0101 and the 2's Complementated Output is Data\_out=1011  
The Input Nibble is Data\_in=0111 and the 2's Complementated Output is Data\_out=1001  
The Input Nibble is Data\_in=0010 and the 2's Complementated Output is Data\_out=1110  
The Input Nibble is Data\_in=1111 and the 2's Complementated Output is Data\_out=0001  
The Input Nibble is Data\_in=0010 and the 2's Complementated Output is Data\_out=1110

- 3) Verilog code for MOD-N up counter with synchronous RESET control, MOD-N down counter with synchronous RESET control, given the value of N. Write relevant Verilog testbenches

### **MOD-N UP Counter (Here MOD Value N is chosen as 8)**

#### **Verilog Code**

```
module modnupcounter(clk,reset,count);
integer i=0;
parameter N=8;/*MOD*/
input clk,reset;
output reg [3:0]count;// Change the Count Size if the N value is greater than 16

always@(posedge clk)
begin
    if(reset)
        begin
            count=0;
        end
    else if(count<N-1)
        begin
            count=count+1;
        end
    else count=4'b0000;
end
endmodule
```



## Testbench

```
module modnupcounter_tb();


reg clk,reset;
wire [3:0]count;// Change the Count Size if the N value is greater than 16

modnupcounter dut(.clk(clk),.reset(reset),.count(count));

initial begin
reset=1'b1;
clk=1'b0;
#8 reset=1'b0;
end

always #5 clk=~clk;
endmodule
```

## OUTPUT WAVEFORM

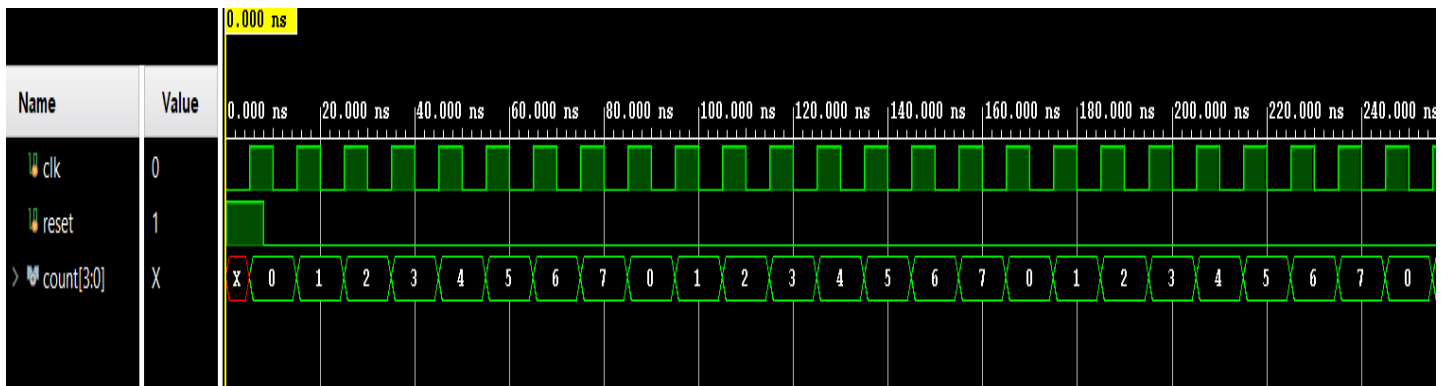

## **MOD N DOWN Counter (Here MOD Value N is chosen as 10)**

### **Verilog Code**

```
module modndowncounter(clk,reset,count);
integer i=0;
parameter N=10;/*MOD*/
input clk,reset;
output reg [3:0]count;// Change the Count Size if the N value is greater than 16

always@(posedge clk)
begin
    if(reset)
        begin
            count=0;
        end
    else if(count>0)
        begin
            count=count-1;
        end
    else count=N-1;
end
endmodule
```

## Testbench

```
module modndowncounter_tb();

reg clk,reset;
wire [3:0]count;// Change the Count Size if the N value is greater than 16


modndowncounter dut(.clk(clk),.reset(reset),.count(count));

initial begin
reset=1'b1;
clk=1'b0;
#8 reset=1'b0;

end

always #5 clk=~clk;
endmodule
```

## OUTPUT WAVEFORM

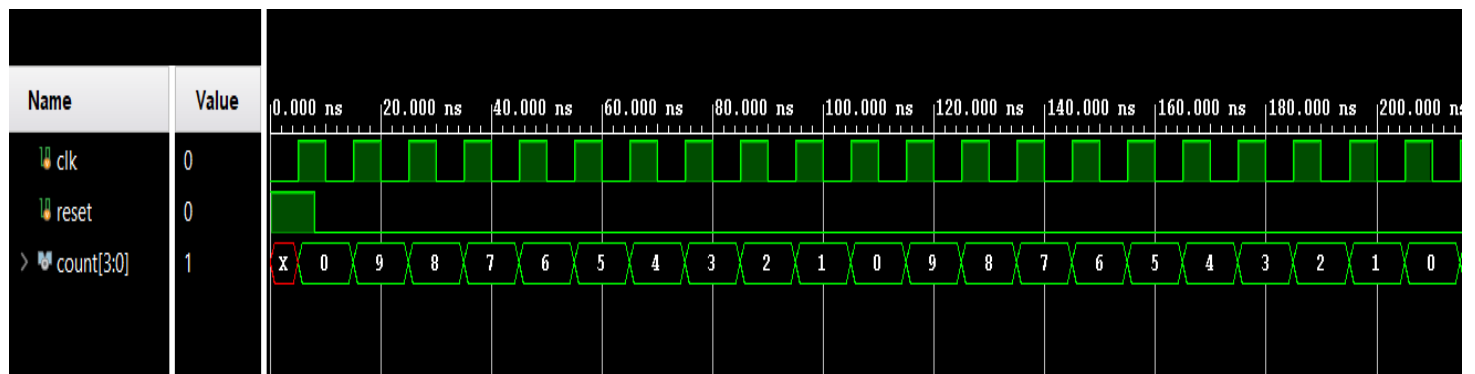

## MOD N UP/DOWN Counter

**Verilog Code** (Here MOD Value N is chosen as 10)

```
module modnupdowncounter(clk,reset,ud,count);
integer i=0;
parameter N=10;/*MOD*/
input clk,reset,ud;//if ud=0 Up Count else down count
output reg [3:0]count;// Change the Count Size if the N value is greater than 16

always@(posedge clk)
begin
    if(reset)
        begin
            count=0;
        end
    else
        if(ud==0)
            begin
                if(count<N-1)
                    count=count+1;
                else count=4'b0000;
            end
        else if(ud==1)
            begin
                if(count>0)
                    count=count-1;
                else count=N-1;
            end
        end

end
endmodule
```

## Testbench

```
module modnupdowncounter_tb();

reg clk,reset,ud;
wire [3:0]count;// Change the Count Size if the N value is greater than 16


modnupdowncounter dut(.clk(clk),.reset(reset),.ud(ud),.count(count));

initial begin
ud=0;
reset=1'b1;
clk=1'b0;
#8 reset=1'b0;
#400 ud=1;
end


always #5 clk=~clk;
endmodule
```

## OUTPUT WAVEFORMS

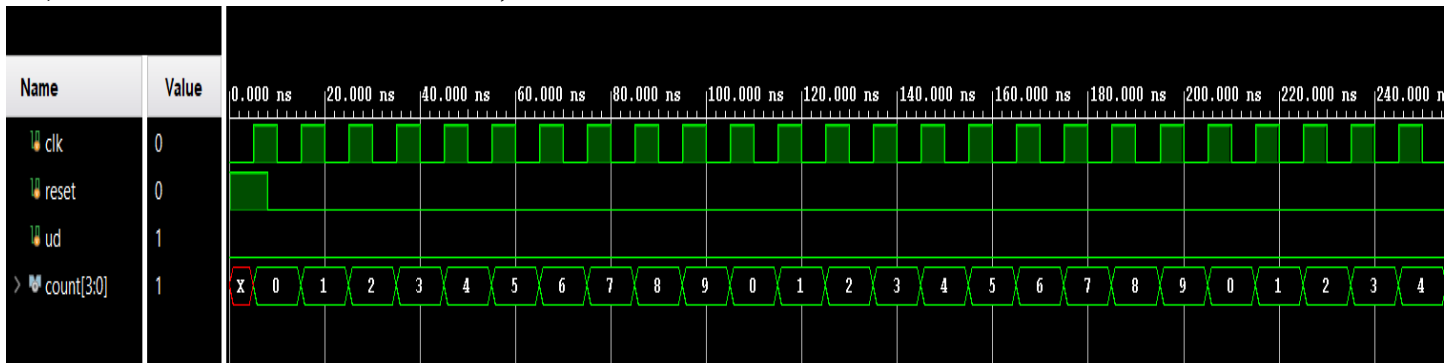
### 1) When ud=0 UP Count , MOD N UP Counter


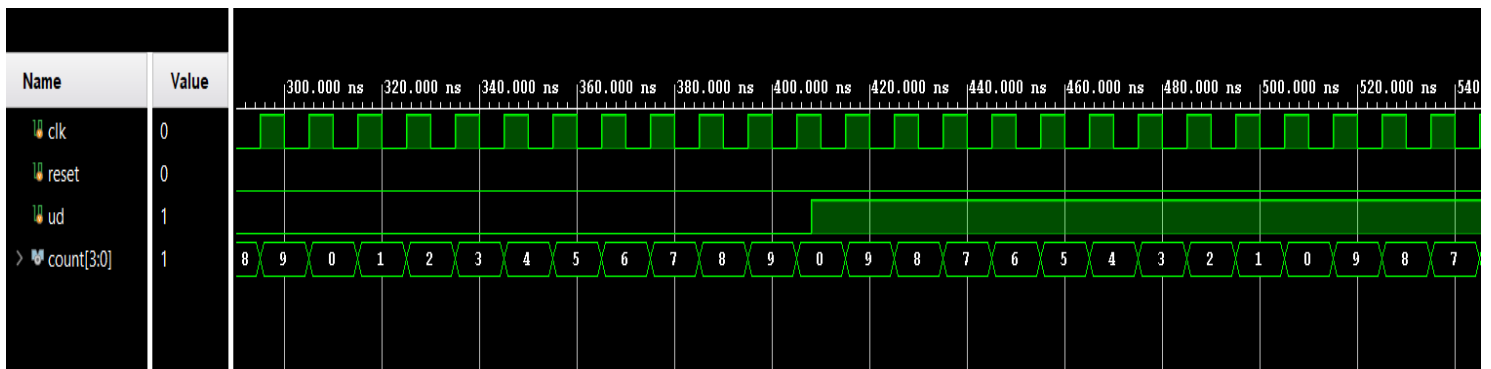
### 2) When ud changes from 0 to 1 Down Count starts


 
### 3) When ud=1, DOWN Count, MOD N DOWN Counter



Github:-

[https://github.com/tusharshenoy/VLSI\\_LAB\\_Practice\\_Questions](https://github.com/tusharshenoy/VLSI_LAB_Practice_Questions)